

Single-Cycle Processor

PROJECT REPORT

Prepared by:

1. Ahmed Mahmoud Abdul-Fattah [CSE].
2. Mahmoud Muhammad Hashem [CSE].
3. Musa Mahmoud Salah [CSE].

Control unit Truth table

<i>Instru ction</i>	<i>Op Code</i>	<i>ALU-F</i>	<i>ALU SRC</i>	<i>A L U O / P</i>	<i>e x t e n d</i>	<i>i m m</i>	<i>RW</i>	<i>MemTo Reg</i>	<i>Reg Dst</i>	<i>Mem Read</i>	<i>Mem Write</i>	<i>R0</i>	<i>S S E T</i>	<i>T E</i>	<i>J</i>	<i>JAL</i>	<i>BEQ</i>	<i>B N E</i>	<i>B</i>
AND	0	AND	0	1	x	x	1	0	0	0	0	0	0	x	0	0	0	0	0
OR	0	OR	0	1	x	x	1	0	0	0	0	0	0	x	0	0	0	0	0
XOR	0	XOR	0	1	x	x	1	0	0	0	0	0	0	x	0	0	0	0	0
EQV	0	EQV	0	1	x	x	1	0	0	0	0	0	0	x	0	0	0	0	0
Add	1	ADD	0	1	x	x	1	0	0	0	0	0	0	x	0	0	0	0	0
Sub	1	Sub	0	1	x	x	1	0	0	0	0	0	0	x	0	0	0	0	0
SLt	1	Slt	0	1	x	x	1	0	0	0	0	0	0	x	0	0	0	0	0
SEQ	1	SEQ	0	1	x	x	1	0	0	0	0	0	0	x	0	0	0	0	0
AndI	4	AND	1	1	1	0	1	0	x	0	0	0	0	x	0	0	0	0	0
ORI	5	OR	1	1	0	0	1	0	x	0	0	0	0	x	0	0	0	0	0
XORI	6	XOR	1	1	0	0	1	0	x	0	0	0	0	x	0	0	0	0	0
EQVI	7	EQV	1	1	0	0	1	0	x	0	0	0	0	x	0	0	0	0	0
AddI	8	ADD	1	1	2	0	1	0	x	0	0	0	0	x	0	0	0	0	0
SLTI	9	Sub	1	1	2	0	1	0	x	0	0	0	0	x	0	0	0	0	0
SEQI	10	Sub	1	1	2	0	1	0	x	0	0	0	0	x	0	0	0	0	0
SLL	11	SLL	1	1	0	0	1	0	x	0	0	0	0	x	0	0	0	0	0
SRL	12	SRL	1	1	0	0	1	0	x	0	0	0	0	x	0	0	0	0	0
ROR	13	ROR	1	1	0	0	1	0	x	0	0	0	0	x	0	0	0	0	0
BEQ	14	Sub	0	0	x	0	0	x	1	0	0	0	0	0	0	0	1	0	0
BNE	15	Sub	0	0	x	0	0	x	1	0	0	0	0	0	0	0	0	1	0
LW	16	Add	1	1	2	0	1	1	x	1	0	0	0	x	0	0	0	0	0
SW	17	Add	1	1	2	0	0	x	1	0	1	0	0	x	0	0	0	0	0
BEQZ	20	Sub	0	0	x	1	0	x	1	0	0	1	0	0	0	0	1	0	1
BNEZ	21	Sub	0	0	x	1	0	x	1	0	0	1	0	0	0	0	0	1	1
BLTZ	22	Sub	0	2	x	1	0	x	1	0	0	1	0	0	0	0	0	0	1
BGEZ	23	Sub	0	2	x	1	0	x	1	0	0	1	0	1	0	0	0	0	1
BGTZ	24	Sub	0	3	x	1	0	x	1	0	0	1	0	0	0	0	0	0	1
BLEZ	25	Sub	0	3	x	1	0	x	1	0	0	1	0	1	0	0	0	0	1
JR	26	Add	0	1	x	1	0	x	1	0	0	1	0	0	0	0	0	0	1
JALR	27	Add	0	1	x	1	1	x	1	0	0	1	0	0	0	1	0	0	1
SET	28	Add	1	1	2	1	1	0	x	0	0	1	0	x	0	0	0	0	0
SSET	29	Add	0	1	0	1	1	0	1	0	0	2	1	x	0	0	0	0	0
J	30	x	x	x	x	2	0	x	x	0	0	x	x	x	1	0	0	0	0
JAL	31	x	x	x	x	2	1	x	x	0	0	x	x	x	1	1	0	0	0

ALU Contol Unit Truth Table for R-type

<i>OpCode</i>	<i>2-bit f</i>	<i>index</i>	<i>ALUoperation</i>	A	B	C	D	E
0	0	0	AND	0	0	0	0	0
0	1	1	OR	0	0	0	0	1
0	2	2	XOR	0	0	0	1	0
0	3	3	EQV	0	0	1	1	1
1	0	4	ADD	0	1	0	0	0
1	1	5	Sub	0	1	0	0	1
1	2	6	Slt	0	1	1	0	1
1	3	7	SEQ	1	0	0	0	1

ALU Contol Unit Truth Table for R-type

<i>OpCode</i>	<i>ALUoperation</i>	A	B	C	D	E
4	AND	0	0	0	0	0
5	OR	0	0	0	0	1
6	XOR	0	0	0	1	0
7	EQV	0	0	0	1	1
8	ADD	0	1	0	0	0
9	Slt	0	1	1	0	1
10	Seq	1	0	0	0	1
11	SLL	0	0	1	0	0
12	SRL	0	0	1	0	1
13	ROR	0	0	1	1	0
14	Sub	0	1	0	0	1
15	Sub	0	1	0	0	1
16	Add	0	1	0	0	0
17	Add	0	1	0	0	0
20	Sub	0	1	0	0	1
21	Sub	0	1	0	0	1
22	Sub	0	1	0	0	1
23	Sub	0	1	0	0	1
24	Sub	0	1	0	0	1
25	Sub	0	1	0	0	1
26	Add	0	1	0	0	0
27	Add	0	1	0	0	0
28	Add	0	1	0	0	0
29	Add	0	1	0	0	0
30	x	x	x	x	x	x
31	x	x	x	x	x	x

Test Code

instruction	Binary Code	Hexadecimal Code
set r1, 0x55	11100 001 0101 0101	E155
sset r1, 0x12	11101 001 0001 0010	E912
sset r1, 0x10	11101 001 0001 0000	E910
sset r1, 0x20	11101 001 0010 0000	E920
sset r1, 0x00	11101 001 0000 0000	E900
set r6, 0x22	11100 110 0010 0010	E622
sset r6, 0x06	11101 110 0000 0110	EE06
sset r6, 0x02	11101 110 0000 0010	EE02
sset r6, 0x11	11101 110 0001 0001	EE11
eqv r3, r6, r1	00000 011 110 001 11	03C7
sub r0,r0,r0	00001 000 000 000 01	0801
lw r1, 0(r0)	10000 001 000 00000	8100
lw r2, 1(r0)	10000 010 000 00001	8201
lw r3, 2(r0)	10000 011 000 00010	8302
addi r4, r4, 10	01000 100 100 01010	448A
sub r4,r4,r4	00001 100 100 100 01	0C91
add r4,r2,r4	00001 100 010 100 0	0628
slt r5,r2,r3	00001 101 010 011 10	0D4E
beq r5,r0,2	01110 101 000 00010	7502
add r2,r1,r2	00001 010 001 010 00	0A28
beq r0,r0,-5	01110 000 000 11011	701B
sw r4, 0(r0)	10001 100 000 00000	8C00
jal func	11111 000 0000 0110	F806
ror r6, r6, 8	01101 110 110 01000	6EC8
lw r4, 1(r0)	10000 100 000 00001	8401
lw r5, 2(r0)	10000 101 000 00010	8502
add r6, r6, r5	00001 110 110 101 00	0ED4
beq r0,r0,-1	01110 000 000 11111	701F
func: sub r0,r0,r0	00001 000 000 000 01	0801
lw r1, 0(r0)	10000 001 000 00000	8100
lw r2, 0(r1)	10000 010 001 00000	8220

lw r3, 1(r1)	10000 011 001 00001	8321
and r4,r2,r3	00000 100 010 011 00	044C
or r5, r2, r3	00000 101 010 011 01	054D
sw r4, 1(r0)	10001 100 000 00001	8C01
sw r5, 2(r0)	10001 101 000 00010	8D02
jr r7	11010 111 0000 0000	D700

$$ALUSRC = (ANDI + ORI + XORI + EQVI + ADDI + SLTI + SEQI + SL + SRL + ROR + LW + SW + SET)$$

$$ALU-Out_{int_0} = (BEQ + BNE + BEQZ + BNEZ + BLTZ + BGEZ) \rightarrow \text{zero bit}$$

$$ALU-Out_{int_2} = (BLTZ + BGEZ + BGTZ + BLEZ) \rightarrow \text{the one bit}$$

$$\text{extender}_0 = ANDI \rightarrow \text{zero bit} \quad \text{extender}_1 = (ADDI + SLTI + SEQI + LW + SW + SET) \rightarrow \text{The one bit}$$

$$\text{immediate}_0 = (BEQZ + BNEZ + BLTZ + BGEZ + BGTZ + BLEZ + JR + JALR + SET + SSET) \rightarrow \text{The zero bit}$$

$$\text{immediate}_2 = (J + JAL) \rightarrow \text{The one bit}$$

$$RW = (BEQ + BNE + SW + BEQZ + BNEZ + BLTZ + BGEZ + BGTZ + BLEZ + JR + J)$$

$$\text{MemToReg} = LW$$

$$\text{RegDST} = (BEQ + BNE + SW + BEQZ + BNEZ + BLTZ + BGEZ + BGTZ + BLEZ + JR + JALR + SSET)$$

$$\text{MemRead} = LW, \text{MemWrite} = SW$$

$$R_0 = (BEQZ + BNEZ + BLTZ + BGEZ + BGTZ + BLEZ + JR + JALR + SET) \rightarrow \text{The zero bit}$$

$$R_0 = SSET \rightarrow \text{The one bit}$$

$$SSET = SSET, TE = (BGEZ + BLEZ), J = (J + JAL), JAL = (JALR + JAL)$$

$$BEQ = (BEQ + BEQZ), BNE = (BNE + BNEZ), JR = JR$$

$$B = (BEQZ + BNEZ + BLTZ + BGEZ + BGTZ + BLEZ + JR + JALR)$$

ALU

Signals

NOT

R

Type

$$ALU-A = SEQI$$

$$ALU-D = (ANDI + ORI + XORI + EQVI + SEQI + SLL + SRL + ROR)$$

$$ALU-C = (SLTI + SLL + SRL + ROR), ALU-d = (XORI + EQVI + ROR)$$

$$ALU-E = \left(ORI + EQVI + SLTI + SEQI + SRL + BEQ + BNE + \right. \\ \left. BEQZ + BNEZ + BLTZ + BGEZ + BGTZ + BLEZ \right)$$


Testing Outputs

File Edit Project Simulation Windows Help



- CPU
- CPU
- Wiring
- Gates
- Plexers
- Arithmetic
- Memory
- Input/Output
- Base
- Register File
- PC Programming
- Instruction Memory
- Control Unit
- 8-bit Extender
- 32-bit ALU

Circuit: CPU	
Circuit Name	CPU
Shared Label	
Shared Label Facing	East
Shared Label Font	SansSerif Plain 12

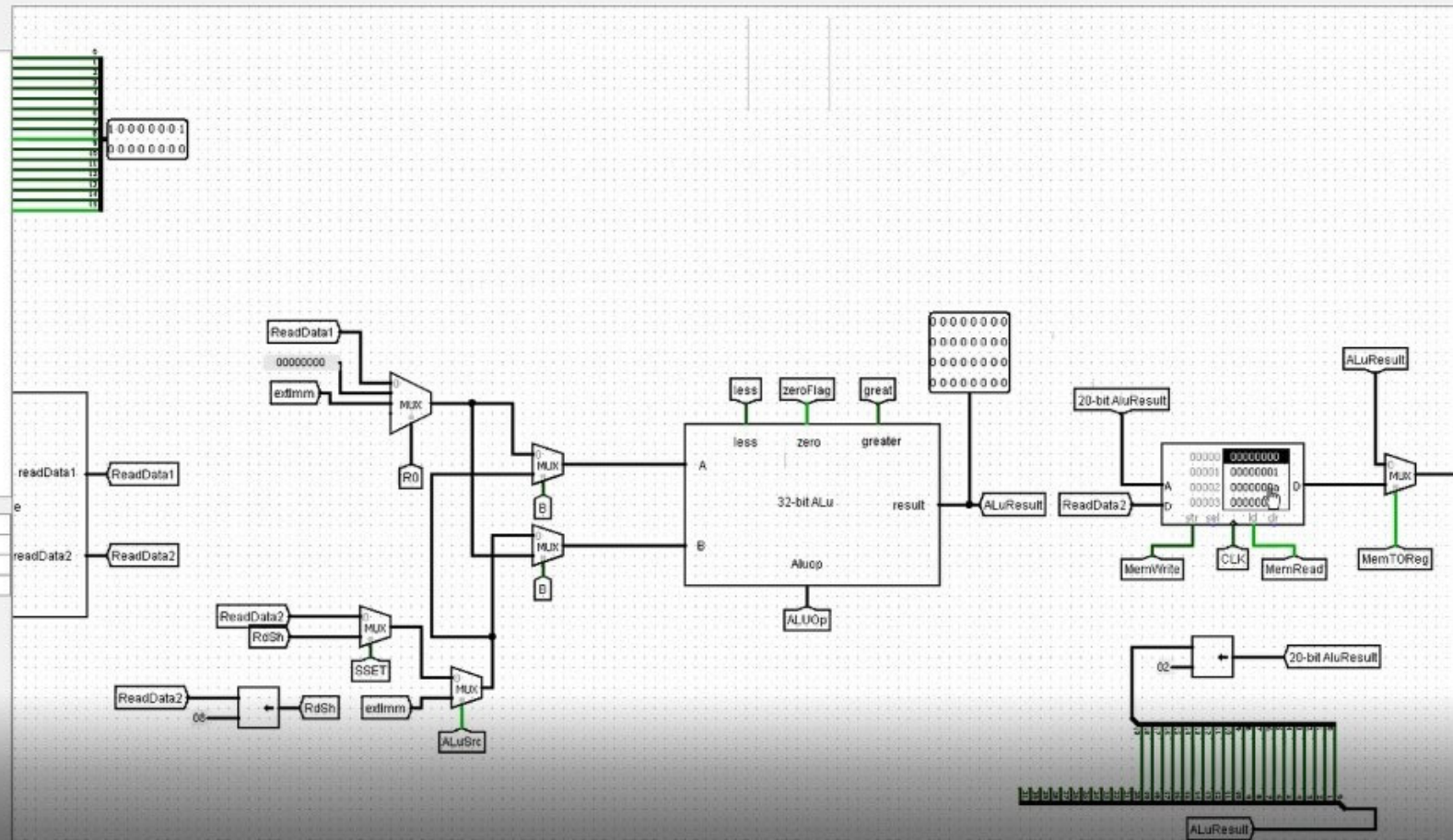


zoom_0

File Edit Project Simulate Window Help



- CPU
- Wiring
- Gates
- Plexers
- Arithmetic
- Memory
- Input/Output
- Base
- Register File
- PC Programming
- Instruction Memory
- Control Unit
- 8-bit Extender
- 32-bit ALU

Circuit: CPU	
Circuit Name	CPU
Shared Label	
Shared Label Facing	East
Shared Label Font	SansSerif Plain 12

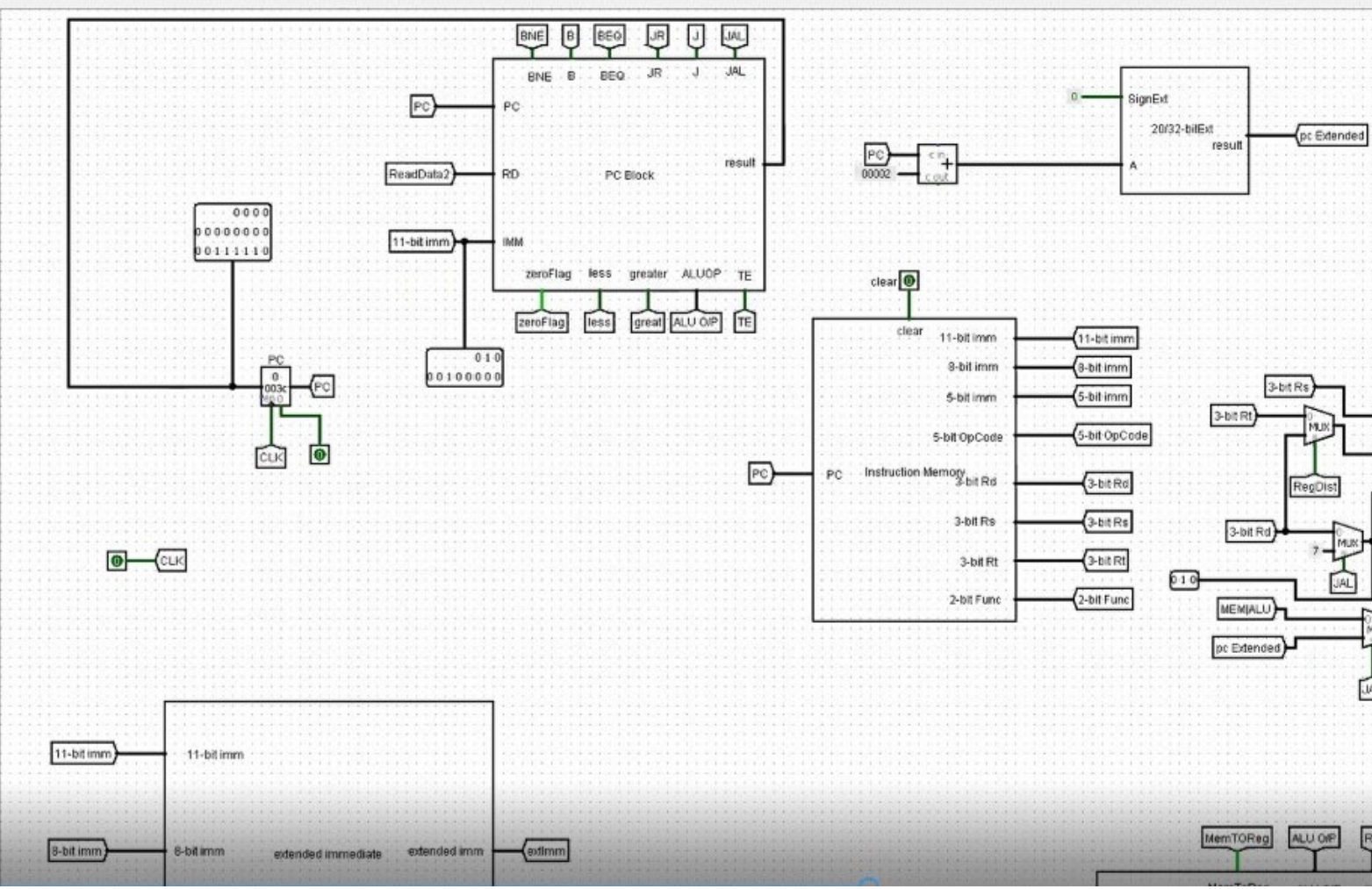



<https://file/d/1RpYQhFzsMsFbKJRbn5bojZFH76RSLkYa/view>

[YouTube](#)
[فيسبوك](#)
[CS50 IDE](#)
[me50/ahmedmamo...](#)
[Android - CS50x](#)

Test Code - Fall_2021.pdf

```

r0,r0,-1 ; program is over, keep looping back to here

```

```
c: sub r0,r0,r0    ; set reg[0] to 0
```

```
r1, 0(r0) ; reg[1] <- mem[0]
```

```
r2, 0(r1) ; reg[2] <- mem[5]
```

```
r3, 1(r1) ; reg[3] <- mem[6]
```

```
r4,r2,r3    ; reg[4] <- reg[2] AND reg[3]
```

```
r5, r2, r3    ; reg[5] <- reg[2] OR reg[3]
```

```
r4, 1(r0) ; mem[1] <- reg[4]
```

```
r5, 2(r0) ; mem[2] <- reg[5]
```

memory starting from address 0 contains:

0]= 00000001

1]=00000001

2]=0000000a

```

3]=00000000

```

```


    ]=00000000


```


55]=430a1f9b

6]=728cd2e3

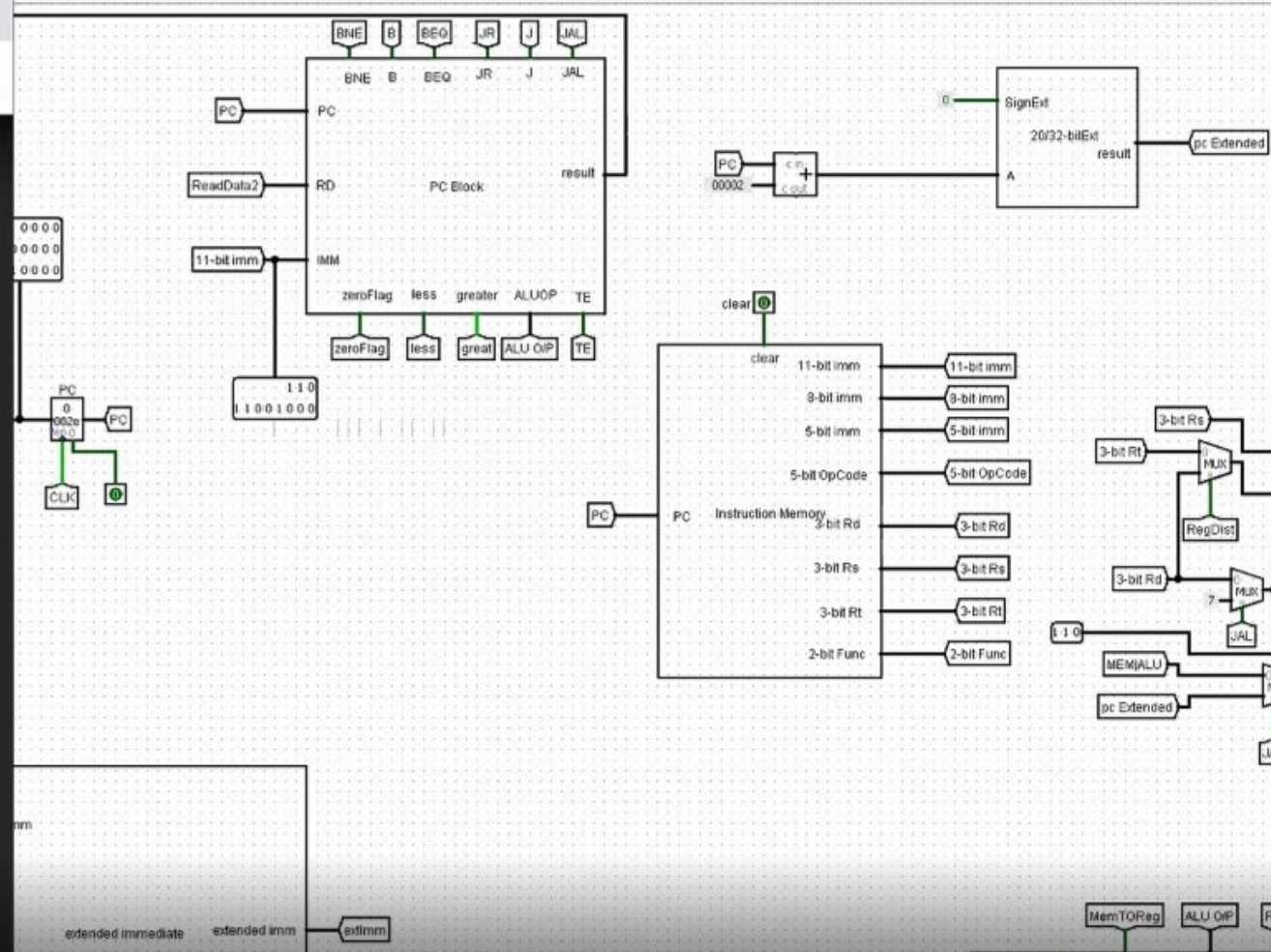
put of all registers and locations of memory that have changed.



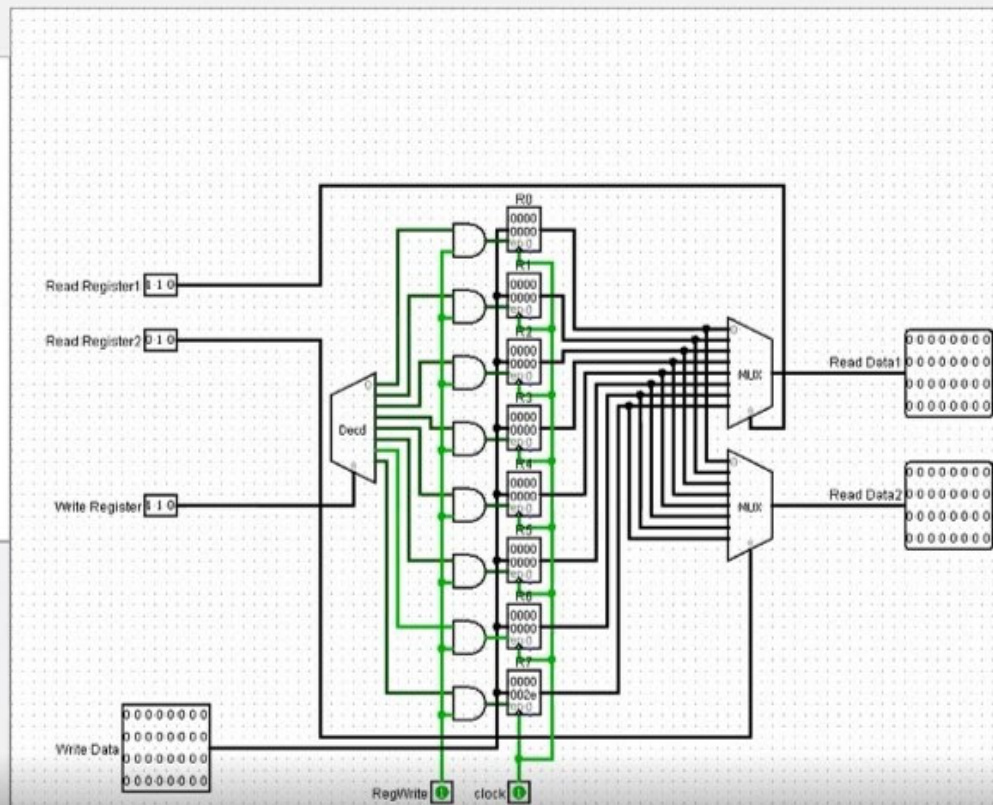

 


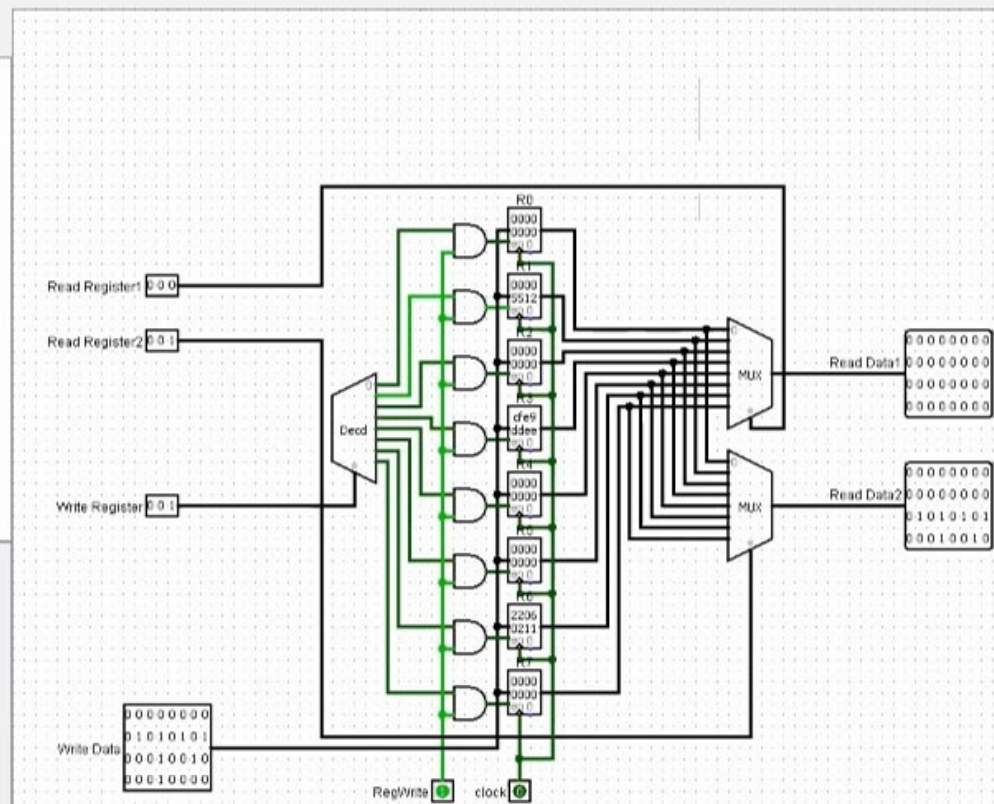- CPU
- Wiring
- Gates
- Muxers
- Arithmetic
- Memory
- Input/Output
- Base
- Register File
- PC Programming
- Instruction Memory
- Control Unit
- 8-bit Extender
- 32-bit ALU






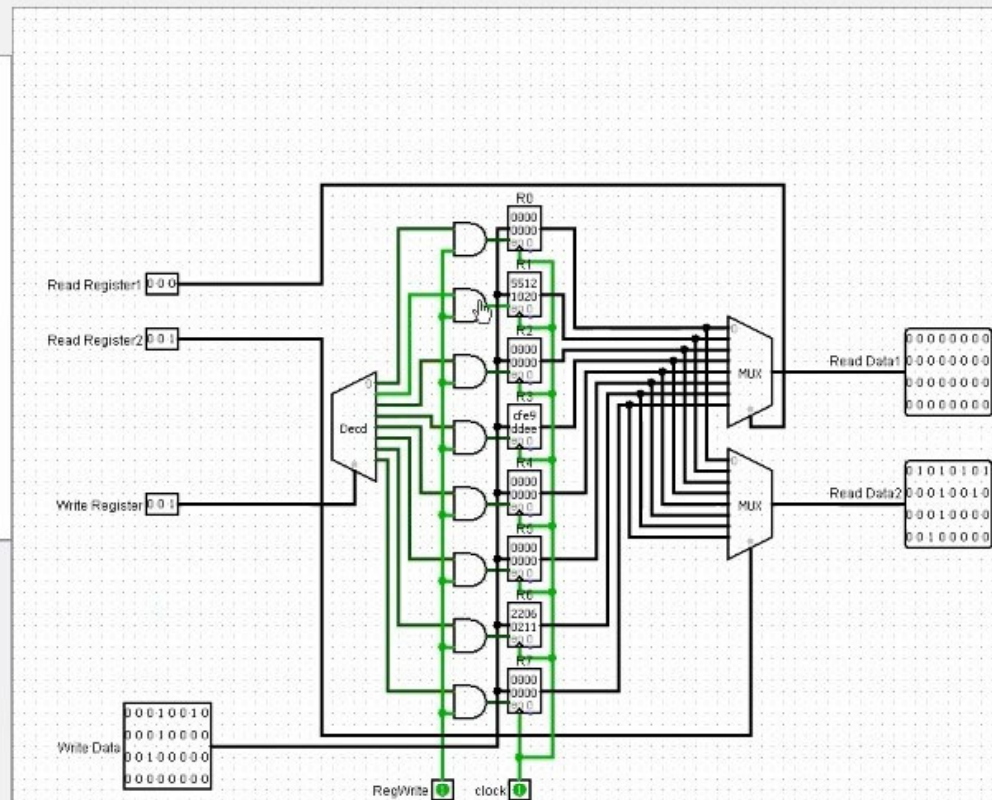- CPU
- Wiring
- Gates
- Multiplexers
- Arithmetic
- Memory
- Input/Output
- Base
- Register File
- PC Programming
- Instruction Memory
- Control Unit
- 8-bit Extender
- 32-bit ALU







 




 - CPU
 - CPU
 - Wiring
 - Gates
 - Plexers
 - Arithmetic
 - Memory
 - Input/Output
 - Base
 - Register File
 - PC Programming
 - Instruction Memory
 - Control Unit
 - 8-bit Extender
 - 32-bit ALU



 


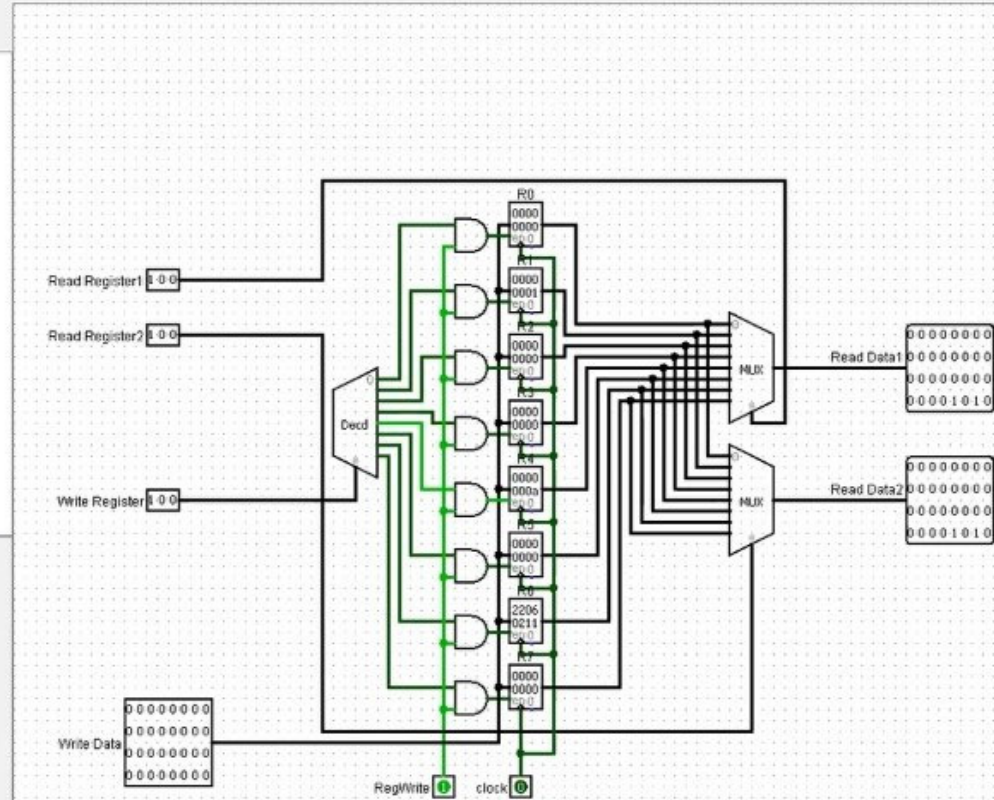
- CPU
- Wiring
- Gates
- Plexers
- Arithmetic
- Memory
- Input/Output
- Base
- Register File
- PC Programming
- Instruction Memory
- Control Unit
- 8-bit Extender
- 32-bit ALU





 - CPU
 - CPU
 - Wiring
 - Gates
 - Plexers
 - Arithmetic
 - Memory
 - Input/Output
 - Base
 - Register File
 - PC Programming
 - Instruction Memory
 - Control Unit
 - 8-bit Extender
 - 32-bit ALU



 

- CPU
- Wiring
- Gates
- Muxers
- Arithmetic
- Memory
- Input/Output
- Base
- Register File
- PC Programming
- Instruction Memory
- Control Unit
- 8-bit Extender
- 32-bit ALU

